

**Due: Sep 10, 2024**  
**Quiz: Sep 12, 2024**  
**Submission: Upload to Canvas**

**Textbook problems:**

1. Problem 1-3 (a, b, c, d)
2. Problem 1-5 (a, b)
3. Problem 1-7 (a, b, c, d, e)

**Boolean functions calculation:**

4. Simplify the following Boolean functions:
  - a.  $F = AB + BC + B'C$
  - b.  $F = A + A'B$
  - c.  $F = A'B'C + A'BC + AB'$
  - d.  $F = AB + (AC)' + AB'C(AB + C)$
  - e.  $F = ((XY' + XYZ)' + X(Y + XY'))'$
5. Obtain the sum of product form of the following functions using Minterms:
  - a.  $F(A, B, C) = A + BC$
  - b.  $F(A, B, C, D) = AB + ACD$
6. Obtain the product of sums form of the following functions using Maxterms:
  - a.  $F(A, B, C) = A + B'C$

**Boolean algebra:**

7. Find the complement of each of the functions by applying DeMorgan's theorem as many times, as necessary:
  - a.  $F1 = X'YZ' + X'Y'Z$
  - b.  $F2 = X(Y'Z' + YZ)$
8. Simplify the following expression using Boolean algebra:
  - a.  $A'BC + AB'C + ABC' + ABC$
  - b.  $(A' + B)' + B(A' + AC) + ABC'$
9. Construct a logic diagram for the given Boolean expressions:
  - a.  $AB + BC(B + C)$
  - b.  $ABC + A(B' + C')$
10. Find the dual of the function,  $F = xyz + x'yz' + y'z$
11. Find the dual of the function,  $F = AB(C + (DL'G(B' + A + E)))(H + (J'A'B))$

**Logic Circuit Implementation:**


12. Implement the function of the following truth table using Sum-of-Products form:

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

13. Implement the function of the following truth table (Output is z) using Sum-of-Products form:

a	b	c	d	z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

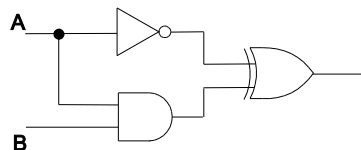14. Show the behavior of the following circuit using a truth table:



15. Show the behavior of the following circuit using a truth table:

